
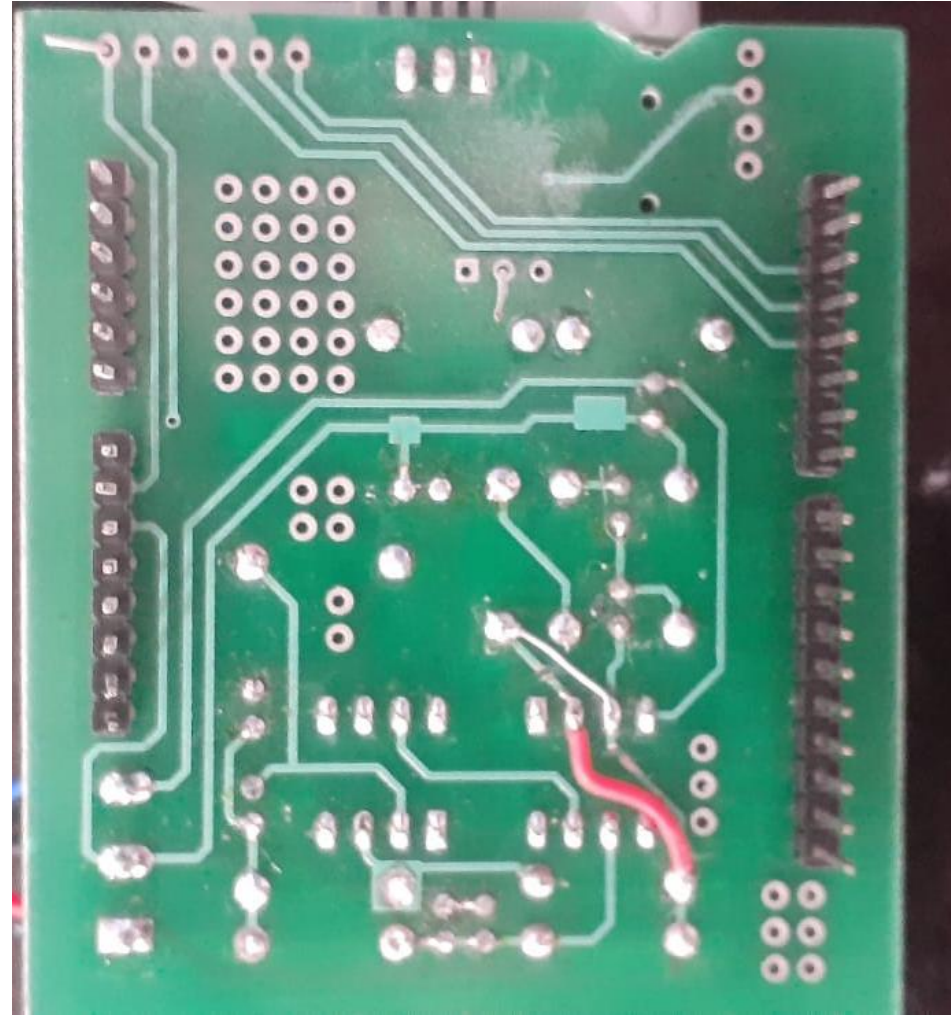


Assembling the BioSignal Amplifier PCB

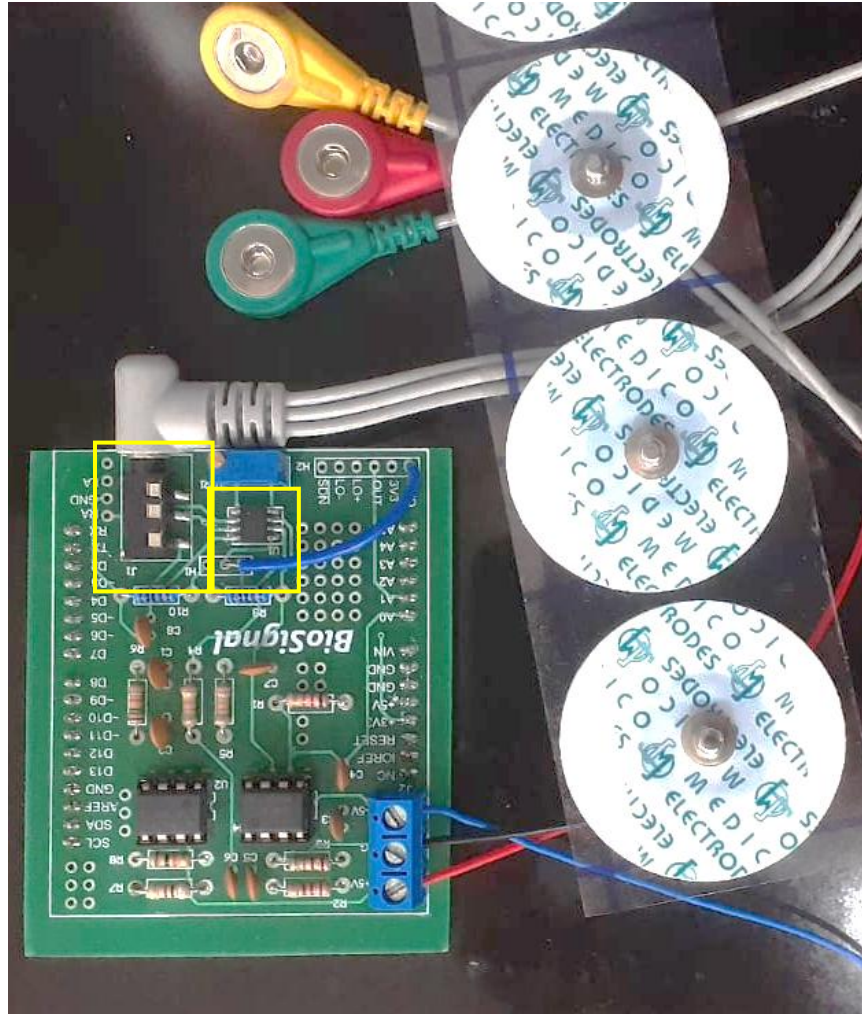

Cables & Connectors





ECG or EMG





EEG

Ideal Notch filter

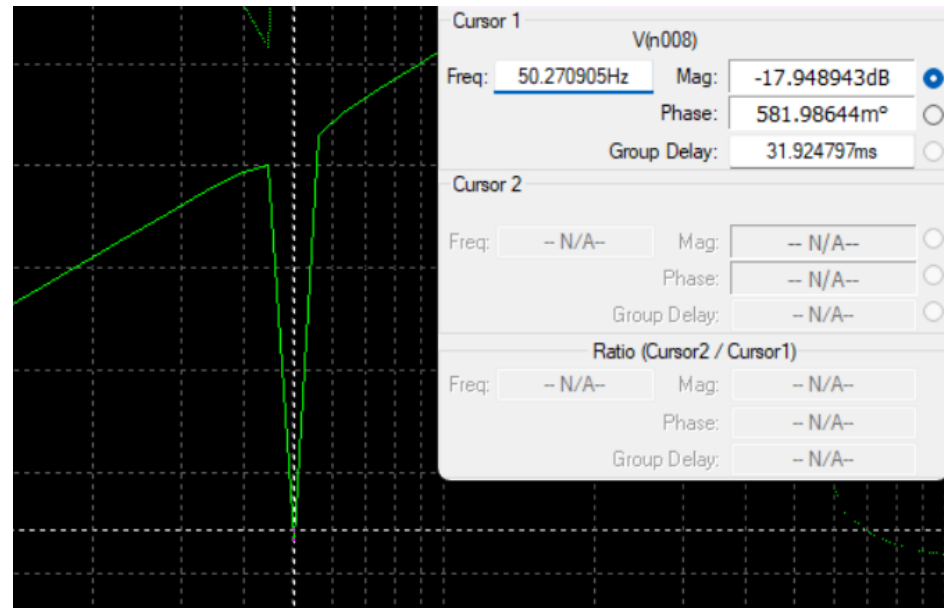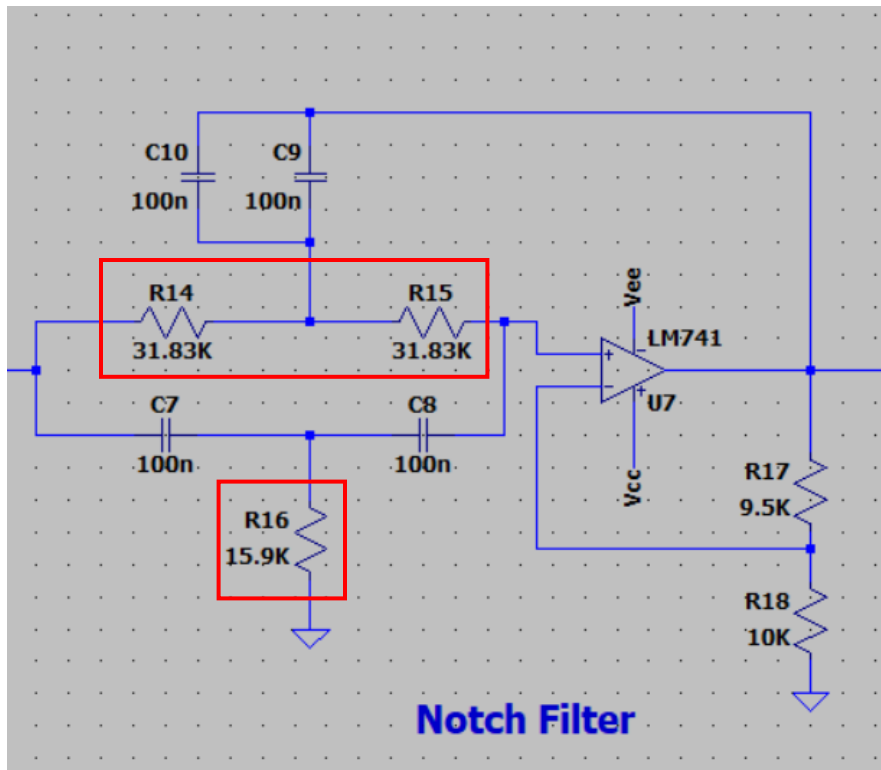

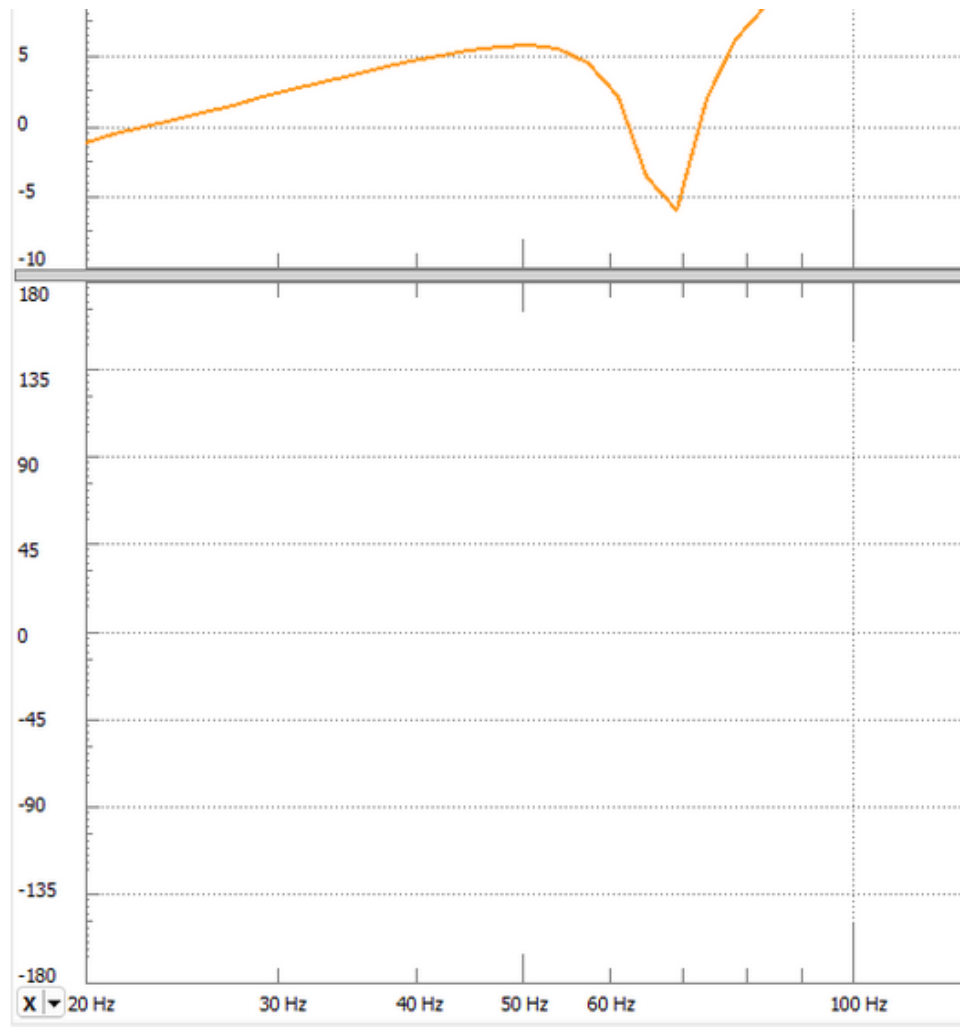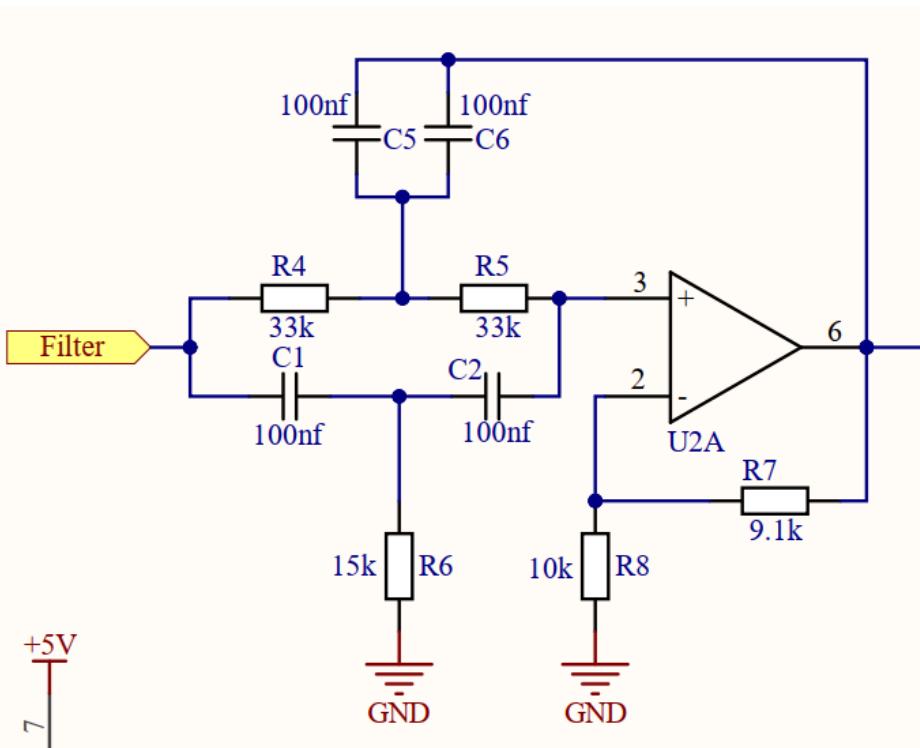
Practical Notch filter using standard resistors



Ideal Bandpass Filter



Design Inputs

#	Name	Cutoff Frequency	326.008 Hz
1.	FilterType	Min GBW Req'd	113.842 kHz
2.	FilterResponse	Stage Gain	3.25 V/V
3.	FilterOrder	Stage Q	1.331
4.	FilterTopology	Stage Topology	Multiple Feedback
5.	NumberOfStag		
6.	CenterFrequen		
7.	StopbandAtten		
8.	PassbandBand		
9.	StopbandBand		
10.	Gain		
11.	DualSupply		
12.	ResistorToleran		
13.	CapacitorToler		

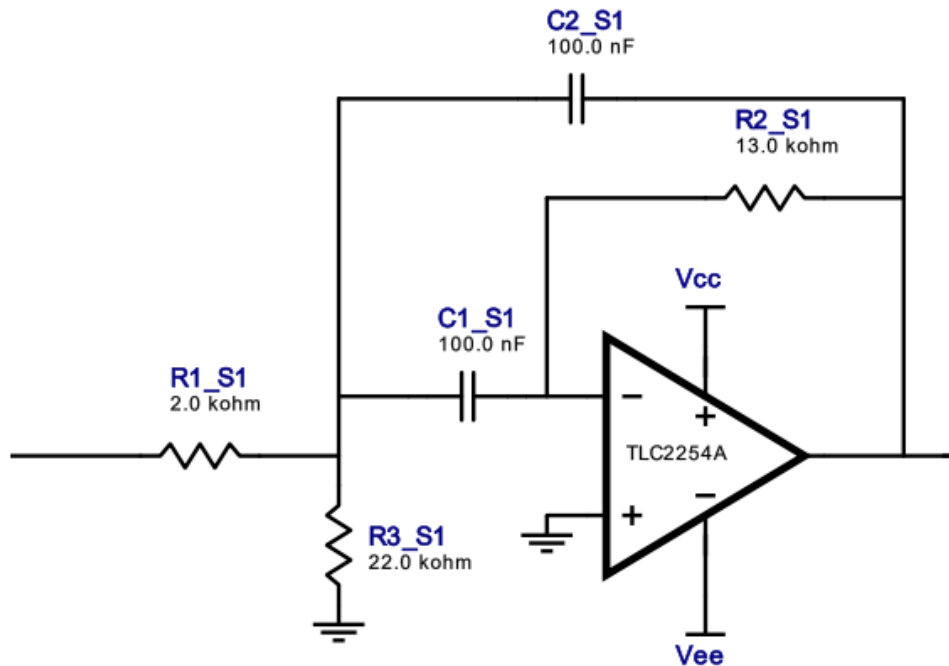

tolerance
tor tolerance

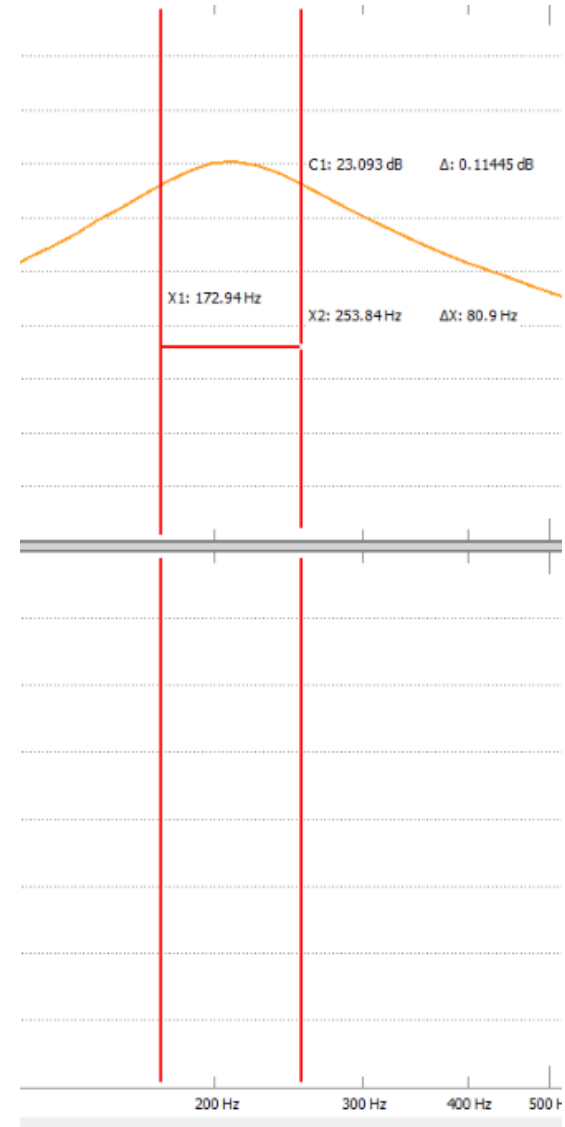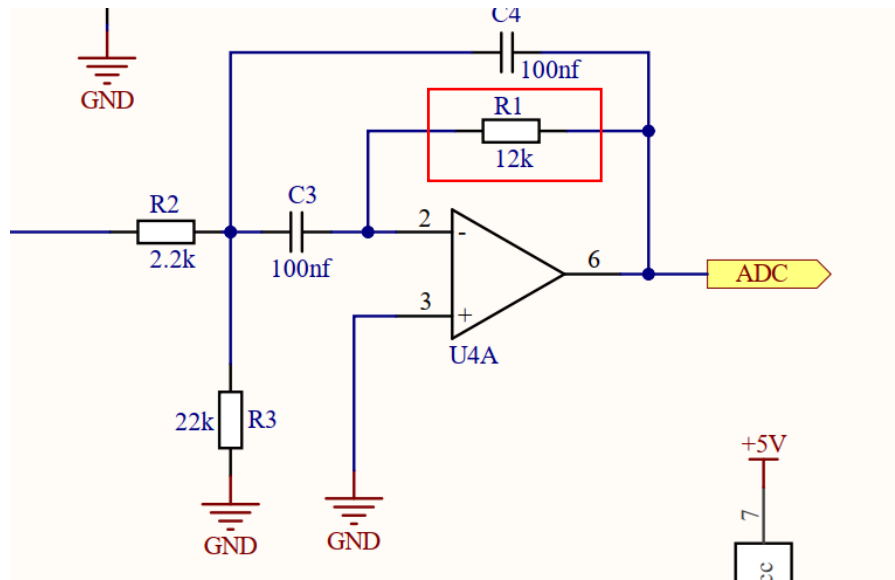Practical Bandpass Filter using standard resistors



Testing BioSignal Amplifier PCB

